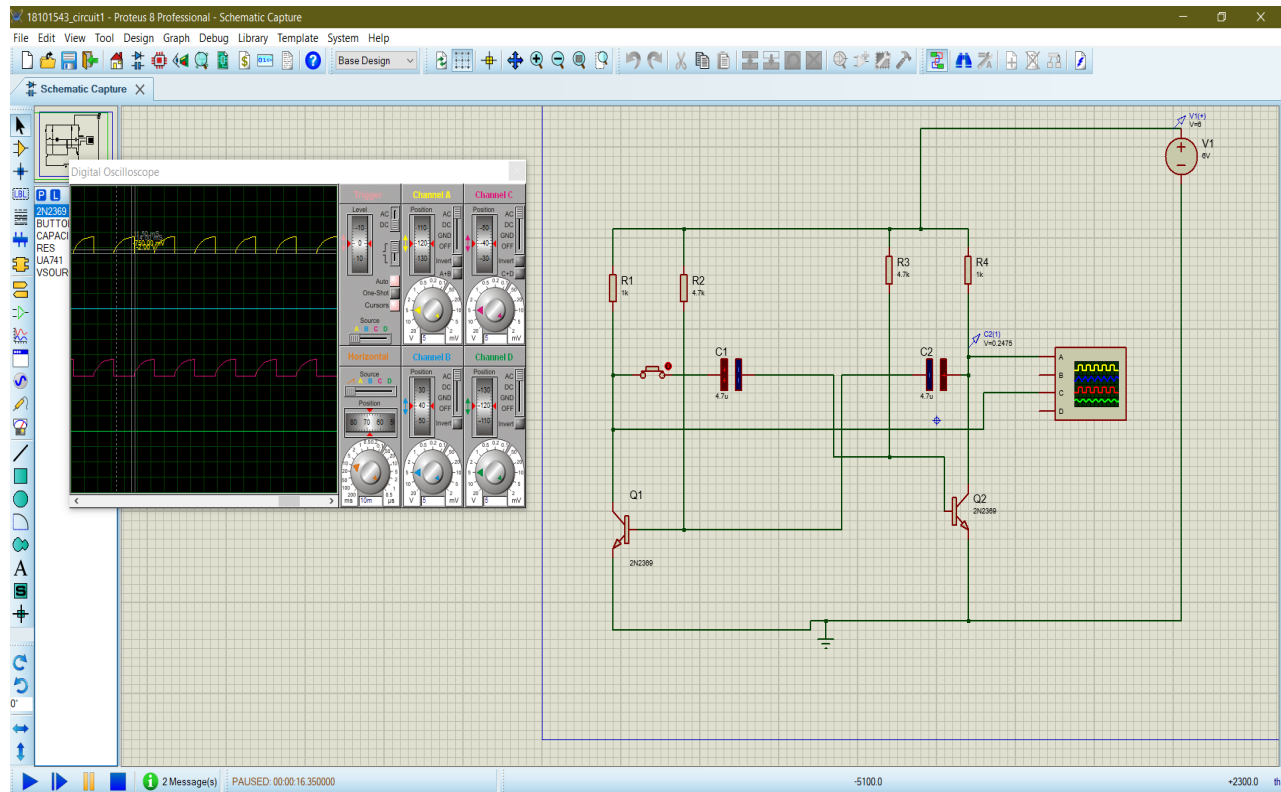





CSE350, LAB06


Submitted by:
Simon Biswas,
Id:18101543
Section: 04.



Ans. to the ques. no. 8 - 01

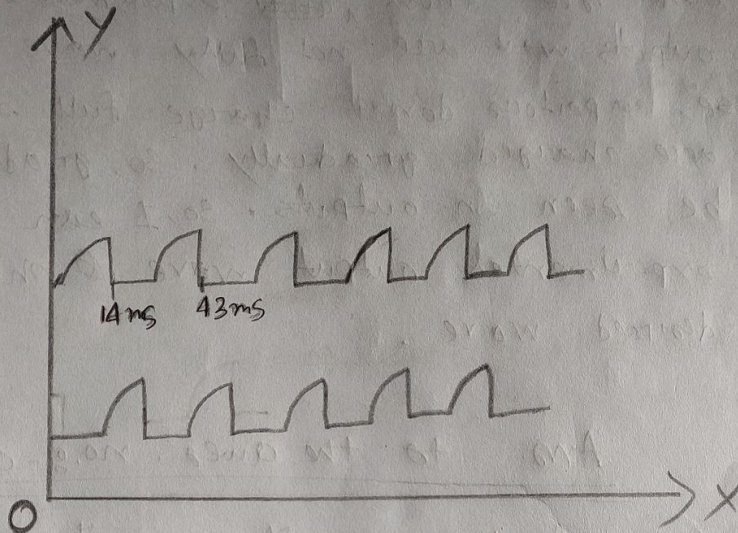

Digital Oscilloscope

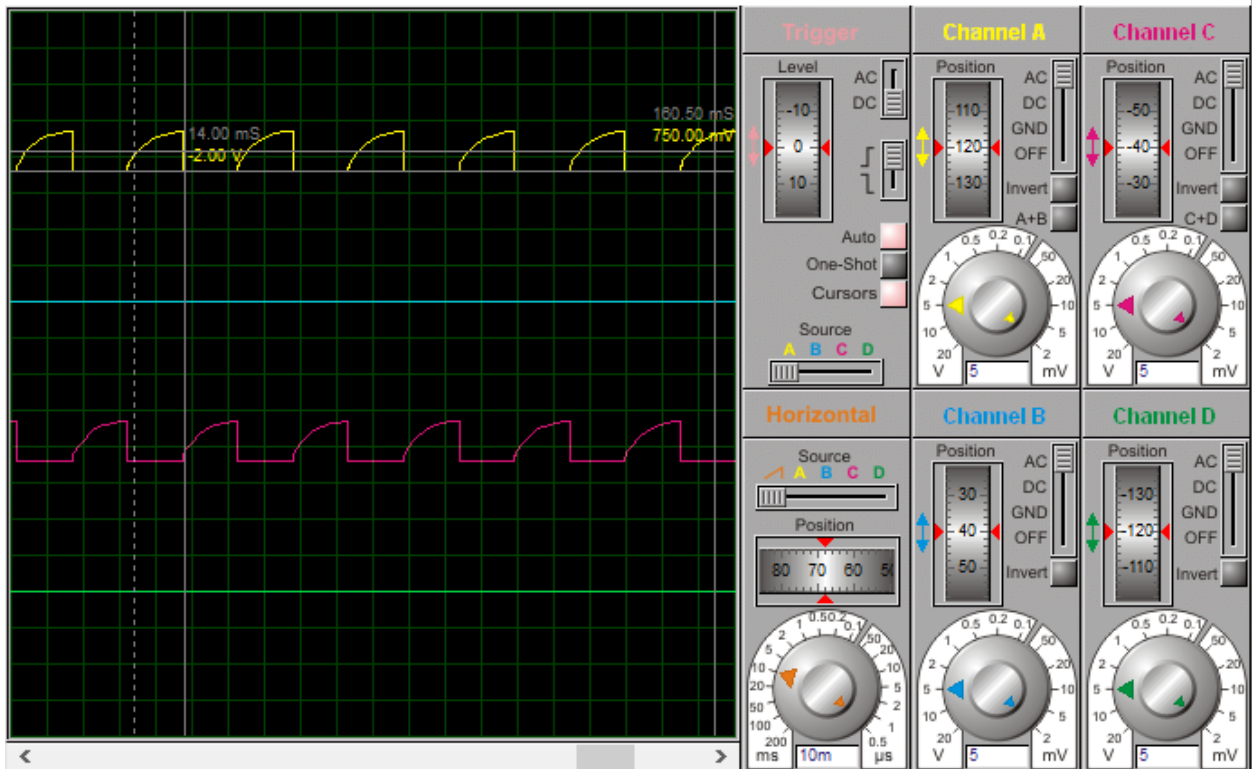

Ans. to the ques. no. 2-02

I ~~can~~ can see from ^{my} ~~our~~ experimental output that outputs ~~wave~~ are not fully wave shaped. Because, capacitors don't charge full suddenly. They are charged gradually. So, gradual changes can be seen in outputs. So, I can see deviation in experimental output wave ~~shape~~ from the desired wave.

Ans. to the ques. no. 2-03

According to theory, if capacitors C_1 and C_2 are same as well as $R_2 = R_3$ then time period $T = 1.38 * R * C$

$$= 1.38 * (4.7 \times 10^3 \Omega) * (4.7 \times 10^{-6} F)$$

$$= 0.030484 s$$

$$= \boxed{30.484 ms}$$

From our experimental output wave we took 2 points to measure time period

point A = 14 ms, point B = 43 ms

$$\text{So, time period} = (43 - 14) = \boxed{29 ms}$$

So, we can see experimental wave is

time period is not exactly same as experimental wave but they are quite similar.

Ans. to the ques no. 2-04

Yes, it is possible to create a variable frequency square wave generator using the given multivibrator. A linear amplifier, a clipping circuit and a π - R differentiating network, connected in regenerative mode, produce discontinuous oscillations. Such a circuit can be successfully used for generating square waves of frequency varying over a fairly wide range.

Ans. to the Ques. no. 2-05

We know, duty cycle = $\frac{t_1}{T} \times 100\%$ where

T = time period

t_1 = high time (on time of the wave)

Here in our experiment $t_1 = t_2$ as capacitors C_1 ~~and~~ C_2 are same and resistors R_2 ~~and~~ R_3 are same. If we change the value of R_2 and C_1 while keeping the C_2 and R_3 as well as $C_1 \neq C_2$, then we can change the duty cycle