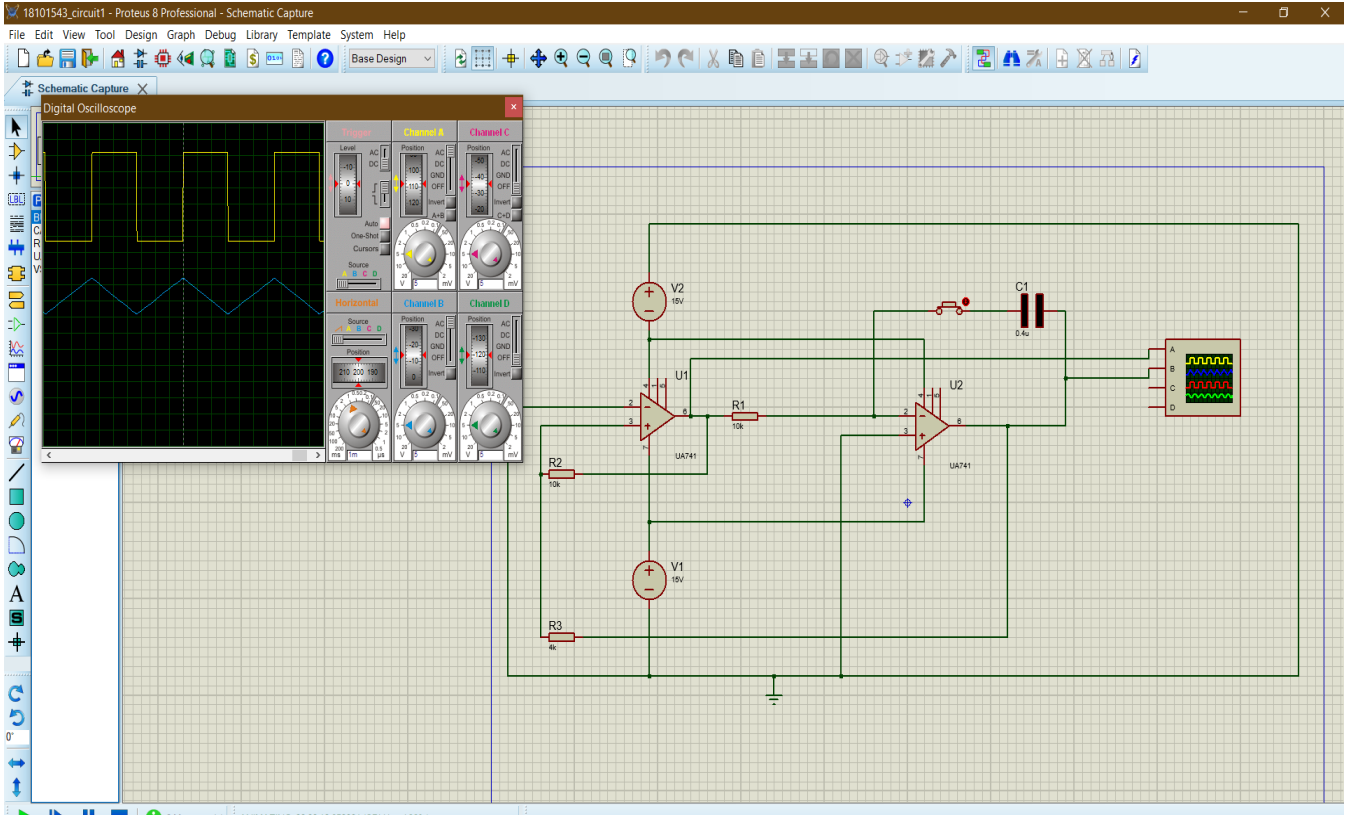




CSE350, LAB05

Submitted by:
Simon Biswas,
Id:18101543
Section: 04.



Theoretical Frequency	Experimental Time Period, T (ms)	Experimental Frequency, F(Hz)
$f = (1/4 * R_1 * C) * (R_2/R_3)$ $= 49.735$	6.5	153.84

Ans. to the Ques. no. 2-01

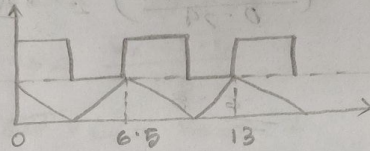


Fig: Output wave shapes.

Ans. to the Ques. no. 2-02

Current flows through R_1 resistor when I_{e1} is in saturation mode. The output of I_{e2} decreases and becomes zero as the capacitor stores charge. When the value of I_{e2} falls below 0, the I_{e1} will become negative. Then current will flow towards I_{e1} through R_1 . The output of I_{e2} stops rising until it reaches ⁱⁿ saturation mode. Again the output of I_{e2} declines after reaching in saturation mode. As a result of this, we see the triangular wave form.

IP-18101543

Ans - to the Ques. no. 8-03

The inductor should not put effect on the experiment. so, the calculation should be same.