

BRAC University  
Department of Computer Science and Engineering  
CSE-350  
EXP-4

**Name of the Experiment:** Analysis of the binary weighted and R/2R ladder D/A converters.


**Objective:**

The objective of this experiment is to construct two different D/A converter and to verify that digital signal is converted into proportional analog signal.

**Equipment:**

Resistance = 10K, 20K, 5K, 2.5K, 1.25K  
Dc source  
Operational Amplifier  
Multimeter


**Op-Amp Device:**

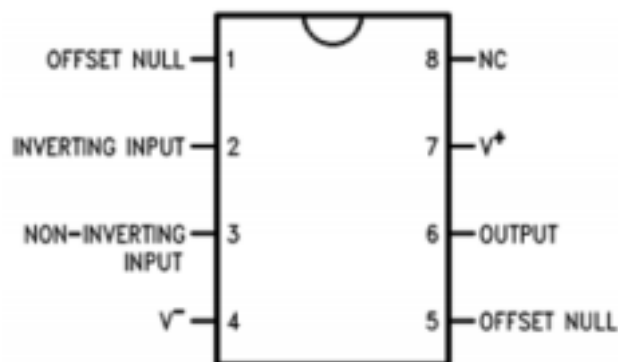

**In case of biasing the operational op-amp,** sort out the positive and negative terminals of two different DC sources. Then connect the rest positive terminal to positive biasing(+V) and the rest negative terminal to negative biasing terminal (-V). The sorted terminal is the ground of the whole circuit. The biasing voltages should be set to +- 15V.

**Circuit Diagram 1:**

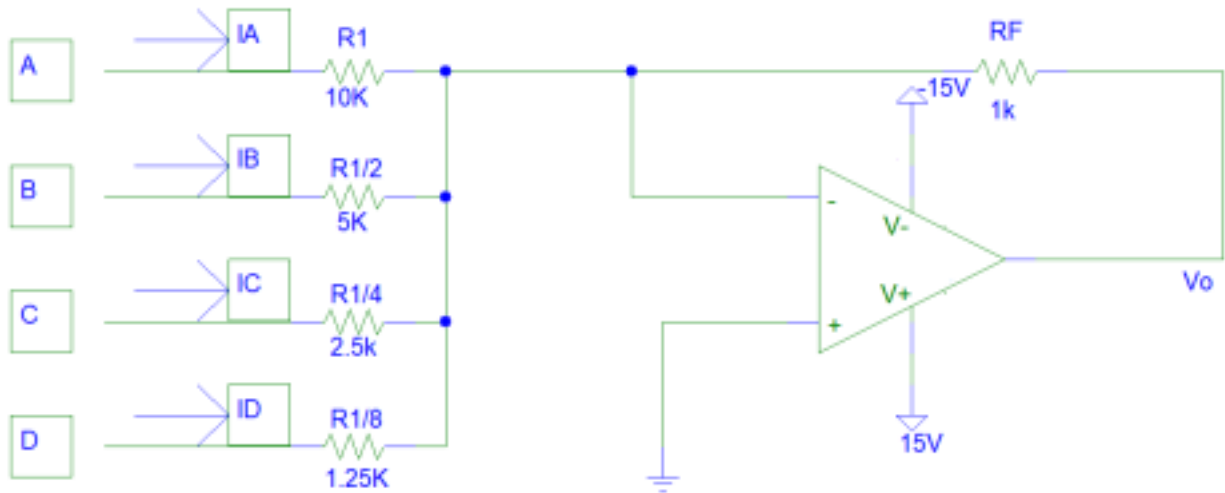**Digital to Analog Converter using Binary-Weighted Resistors**



### Theory:

A four bit converter will have  $2^4 = 16$  input combinations. Consequently, the converter will show 16 different output analog voltage levels for 16 of the different combinations.

### Working Principle:

#### Case 1: A=1 and B=C=D=0:

The voltage across R1 is 5V. So, the current through R1 is  $I_A = 0.5\text{mA}$ . Since the current into the op-amp input terminals are negligible, this 0.5mA current will flow through the  $R_F$  resistance. Hence, the voltage across the resistance  $R_F$  is,

$$V_{RF} = 0.5\text{mA} * 1\text{K} = 0.5\text{V}$$

Consequently, the output voltage is at -0.5V.

#### Case 2: B=1 and A=C=D=0:

The voltage across R1/2 is 5V. So, the current through R1/2 is  $I_B = 1\text{mA}$ . Since the current into the op-amp input terminals are negligible, this 1mA current will flow through the  $R_F$  resistance. Hence, the voltage across the resistance  $R_F$  is,

$$V_{RF} = 1\text{mA} * 1\text{K} = 1\text{V}$$


Consequently, the output voltage is at -1V.

#### Case 3: A=B=1 and C=D=0:

The voltage across R1 is 5V and the voltage across R1/2 is 5V. The current through R1 is  $I_A = 0.5\text{mA}$  and the current through R1/2 is  $I_B = 1\text{mA}$ . So, the total current through the resistance  $R_F$  is 1.5mA. Hence, the voltage across the resistance  $R_F$  is,

$$V_{RF} = 1.5\text{mA} * 1\text{K} = 1.5\text{V}$$

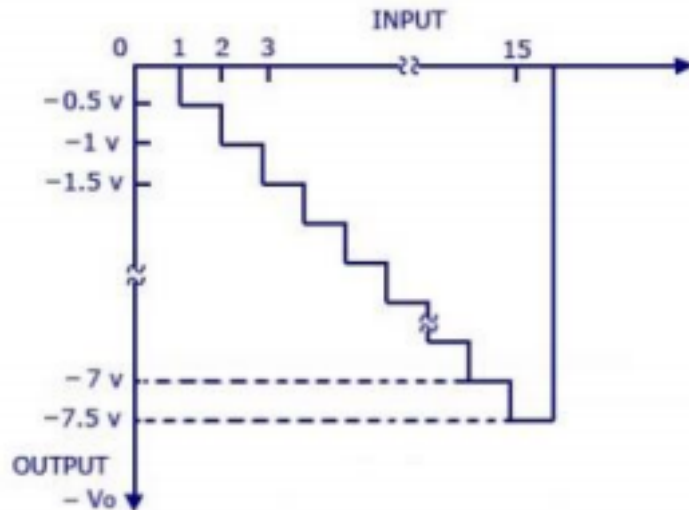Similarly, consider other cases where all possible cases are experimented. The output voltage levels corresponding to input voltage levels are varying as in the figure.




The output is a negative going staircase waveform with 15 steps of -0.5V each. In practice, due to the variations in the logic HIGH voltage levels, all the steps will not have the same size. The value of the feedback resistor  $R_F$  changes the size of the steps. Thus, a desired size for a step can be obtained by connecting the appropriate feedback resistor. The only condition to look out for is that the maximum output voltage should not exceed the saturation levels of the op-amp.

## Circuit Diagram 2:

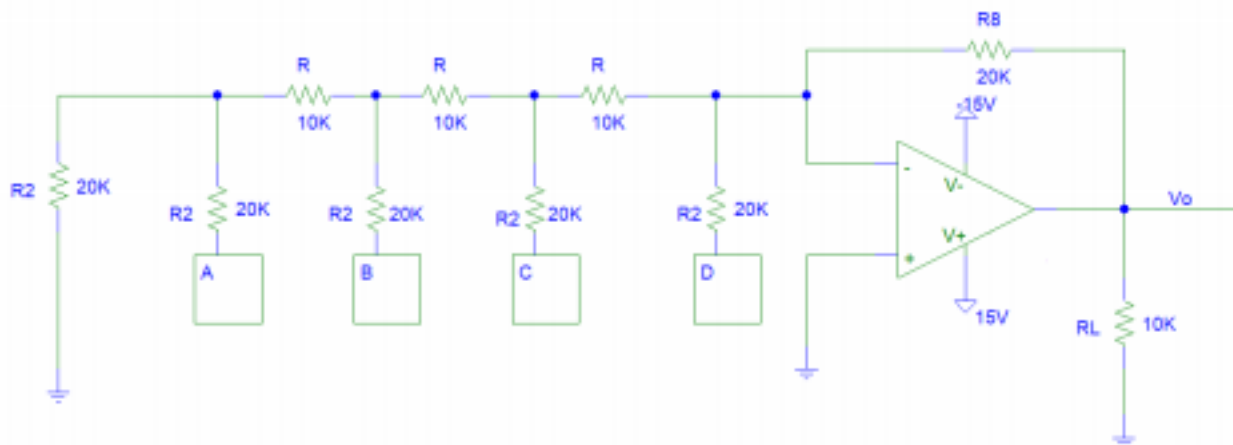
### Digital to Analog Converter with R and 2R Resistors

A D/A converter with R and 2R resistors is shown in the figure below. As in the binary-weighted resistors method, the binary inputs are simulated by the switches A-D and the output is proportional to the binary inputs. Binary inputs can be either in the HIGH (+5V) or LOW (0V) state.



The circuit can be solved using thevenin theorem. The graph with the analog outputs versus

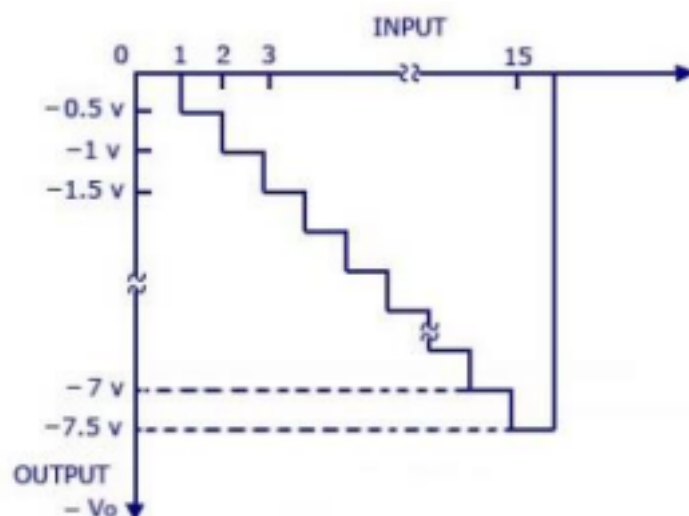possible combinations of inputs is shown below.



### Procedure:

1. Construct the circuits on the trainer board. Supply +15V and -15V to the opamp.
2. The High input is 5V and the low input is 0V.
3. Use multimeter to measure the output magnitude varied with the input signals. This is the analog signal output. Make a table and take data for all possible combinations.

### Report:

1. Can you get output higher than 15V in D2A converters? if so, how?
2. What is the full step output for both D2A converters?
3. What is the resolution?
4. What will be the analog output for the above circuit if the high input voltage is the sum of the last two digits of your Student ID number and the low input is zero? Draw a table and fill up it for all possible input combinations.
5. How does the step size vary with respect to  $R_F$  (feedback resistance)?

(reports must include input output graphs of both D2A converters)

### Datasheet for circuit 1:

Input Configuration	D	C	B	A	Output Voltage, $V_o$ (V)
1					

2					
3					
4					
5					
6					
7					
8					
9					
10					
11					
12					
13					
14					
15					
16					

**Datasheet for circuit 2:**

Input Configuration	D	C	B	A	Output Voltage, $V_o$ (V)
1					
2					
3					
4					

5					
6					
7					
8					
9					
10					
11					
12					
13					
14					
15					
16					