



CSE350, LAB01

Submitted by:


Simon Biswas,

Id:18101543

Section: 04.


OR Gate(Figure 01) :

VA	VB	VR1	VR2	IR1	IR2	VR=Y
5	5	0.01	0.01	0.000022	0.000022	4.57
0	5	0.00	0.02	0	0.000044	4.536
5	0	0.02	0.00	0.000044	0	4.536
0	0	0.00	0.00	0	0	5.57101e-01 1/0.00

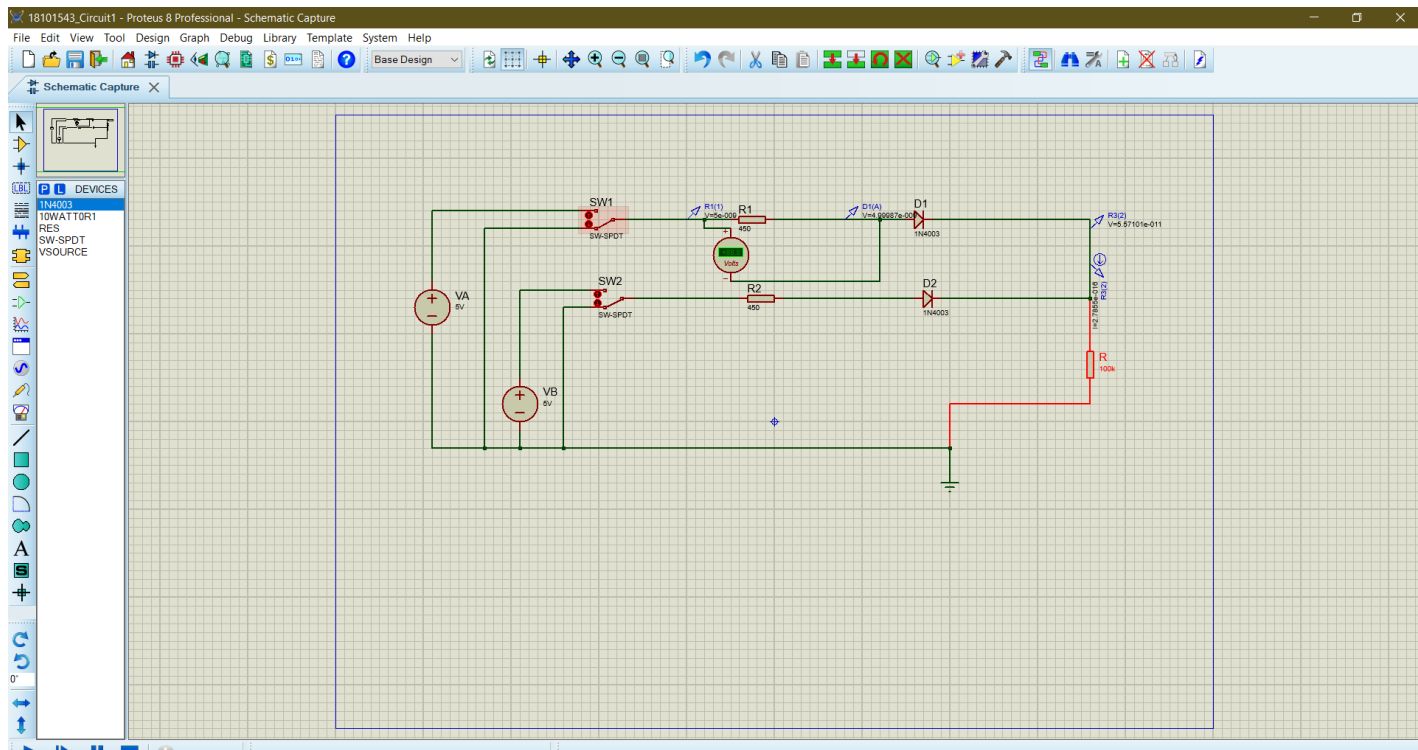


AND Gate(Figure 02):

VA	VB	VR1	VR2	IR1	IR2	VR=Y
5	5	0.00	0.00	0.00	0.00	5
0	5	0.02	0.00	0.000044	0.00	0.463
5	0	0.00	0.02	0.00	0.000044	0.463
0	0	0.01	0.01	0.000022	0.000022	0.42229

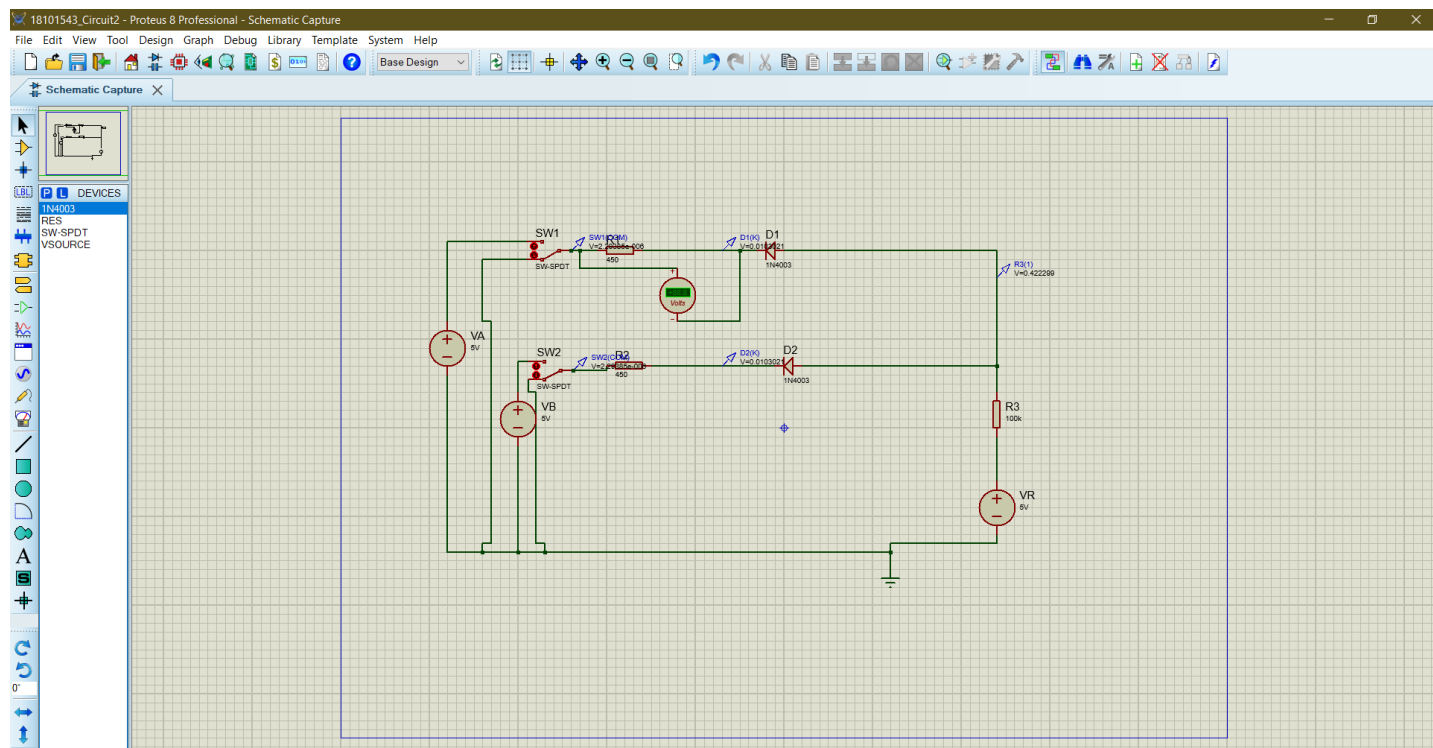

Inverter(Figure 03):

Vi	VR1	VR2	VRC	I1	I2	IB	IC	Y
5	4.30	5.70	4.89	0.28	0.05	0.23	2.22	0.108118
0	0.65	4.35	0	0.04	0.04	0.0	0	5

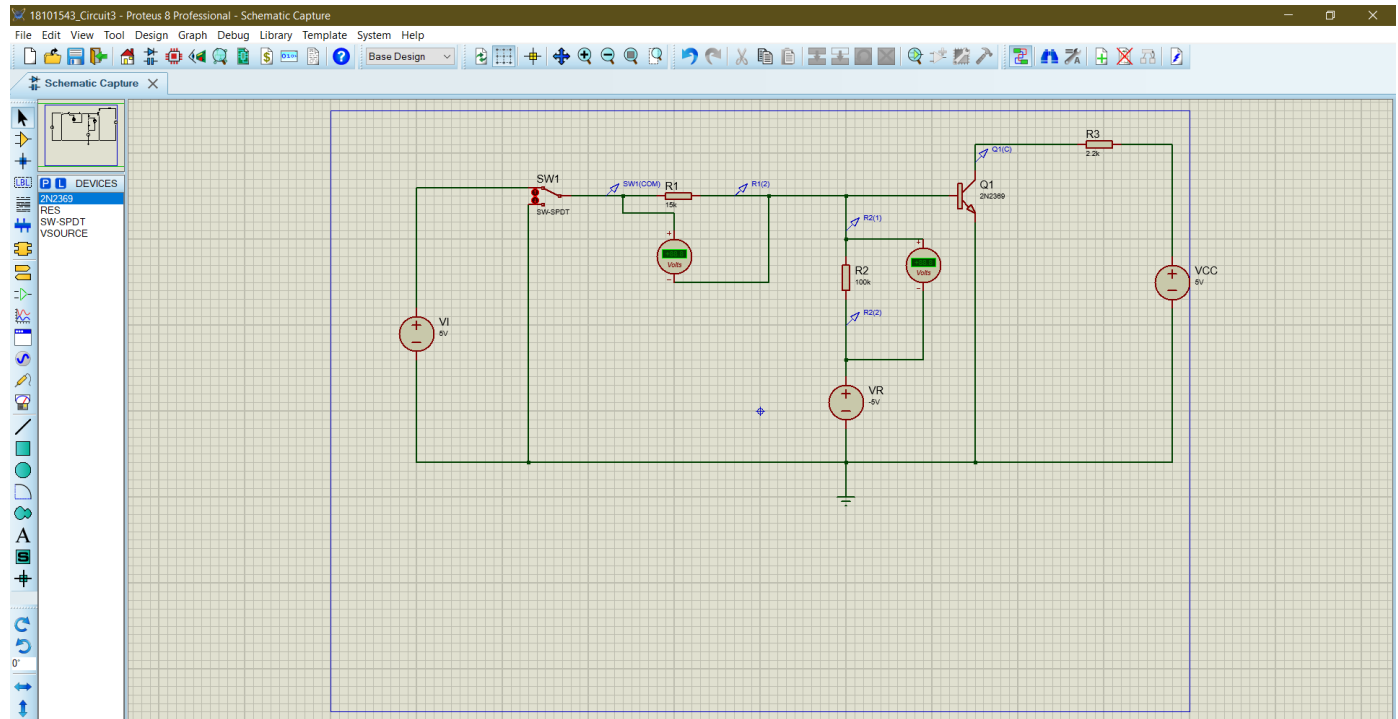

ID-18101543

① What happens if not all inputs have the same upper levels?

⇒ For OR gate: When all the inputs are ~~not~~ in lower level the output becomes 0. If one or more inputs are in high level then output becomes 1.

For AND gate: If all the inputs are in lower level output becomes 0. If any of the input is in lower level, output will be 0. But if all the inputs ~~have~~ are in high level then output will be 1.

② Will the diode D_1 and D_2 will work, if $V_A = V_B = 6V$ and $V_R = 5V_0$

⇒ By using potentials we can see if we use $V_A = V_B = 6V$ and $V_R = 5V$ the diode will be in reverse bias mode. ~~The~~

ID-18101543

② What is the function of $R_2 = 10\Omega$ at the base of an inverter in figure 39?

⇒ It helps to ~~reduce~~ ^{flow} produce a less amount of current in the case of I_1 and I_2 so that more current can pass through I_B .

ID-18101543

① Verify that the transistor will be operating in the saturation and cutoff region in two cases for the inverter circuit.

⇒ From data, I've got from proteus,
when $V_i = 5V$ (ON)

$$I_B = 0.23A > 0$$

$$I_E = 2.22A > 0$$

$$\text{output voltage} = 0.108 \approx 0V$$

$$V_{BE} = 0.7V$$

$$\text{We know, } I_E = I_B + I_C = 0.23 + 2.22 \\ = 2.45A > 0$$

So, the inverter is in saturation mode

when $V_i = 0V$ (OFF)

$$I_B = 0A$$

$$I_C = 0A$$

$$\text{So, } I_E = I_B + I_C = 0A$$

$$\text{So, } I_E = I_B = I_C = 0A$$

$$V_{BE} < 0$$

So, it is in cutoff mode.

ID-18101543.

⑤ What is the function of $-5V$ voltage source in the inverter circuit?

⇒ When $V_i = 0V$ that time $-5V$ helps the inverter not to go in reverse bias mode. No current pass through the base. We only get I_1 and I_2 . As no current flow through the base, the inverter remains in cutoff mode.