



**CSE350, LAB04**

**Submitted by:**


Simon Biswas,

Id:18101543

Section: 04.


**Datasheet for circuit 1:**

Configuration	D	C	B	A	Output Voltage, $V_o$ (V)
1	0	0	0	0	-0.0027
2	0	0	0	5	-0.49
3	0	0	5	0	-0.99
4	0	0	5	5	-1.49
5	0	5	0	0	-1.99
6	0	5	0	5	-2.49
7	0	5	5	0	-2.99
8	0	5	5	5	-3.49
9	5	0	0	0	-3.99
10	5	0	0	5	-4.49
11	5	0	5	0	-4.99
12	5	0	5	5	-5.49
13	5	5	0	0	-5.99
14	5	5	0	5	-6.49
15	5	5	5	0	-3.49
16	5	5	5	5	-7.49

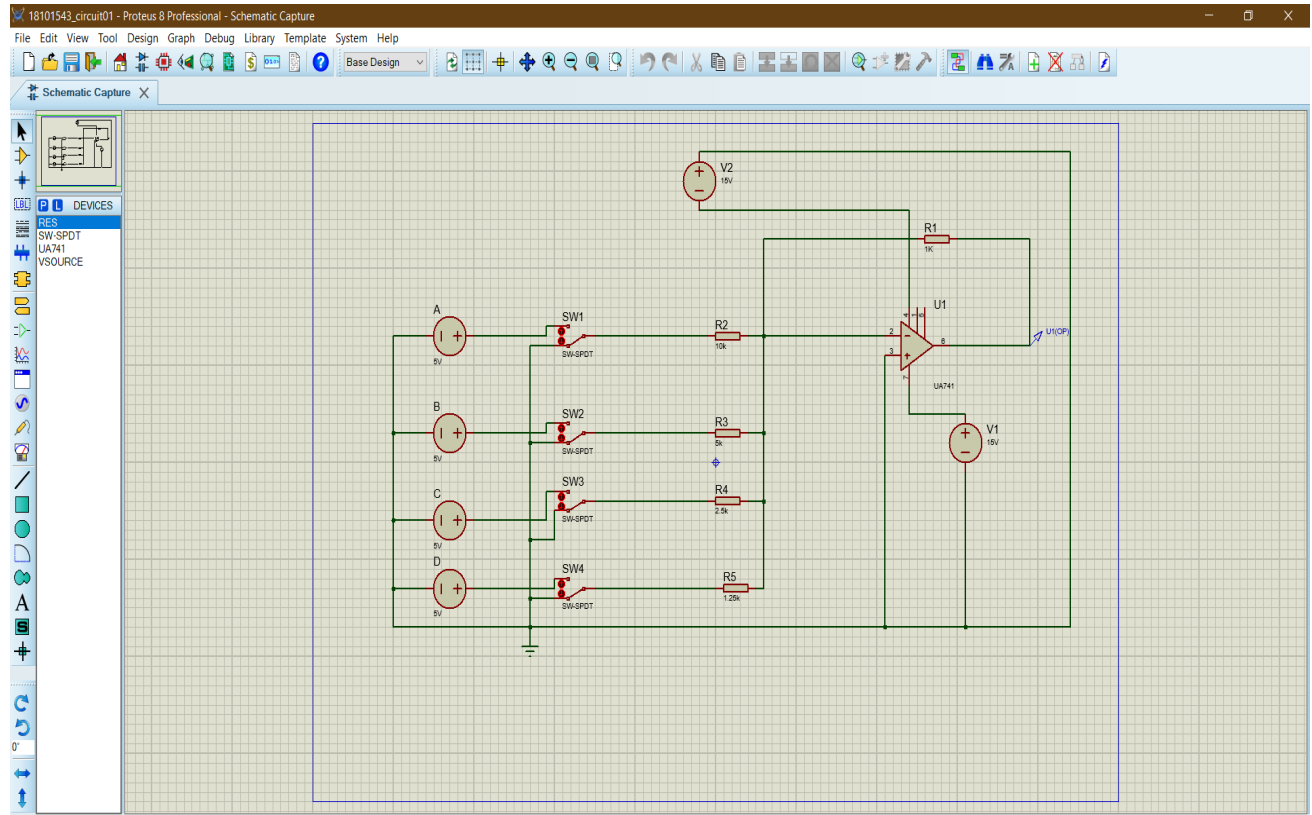

**Datasheet for circuit 2:**

Configuration	D	C	B	A	Output Voltage, $V_o$ (V)
1	0	0	0	0	0.0049
2	0	0	0	5	-0.62
3	0	0	5	0	-1.245
4	0	0	5	5	-1.869
5	0	5	0	0	-2.49
6	0	5	0	5	-3.11
7	0	5	5	0	-3.74
8	0	5	5	5	-4.36
9	5	0	0	0	-4.99
10	5	0	0	5	-5.81
11	5	0	5	0	-6.24
12	5	0	5	5	-6.86
13	5	5	0	0	-7.49
14	5	5	0	5	-8.11
15	5	5	5	0	-8.74
16	5	5	5	5	-9.36

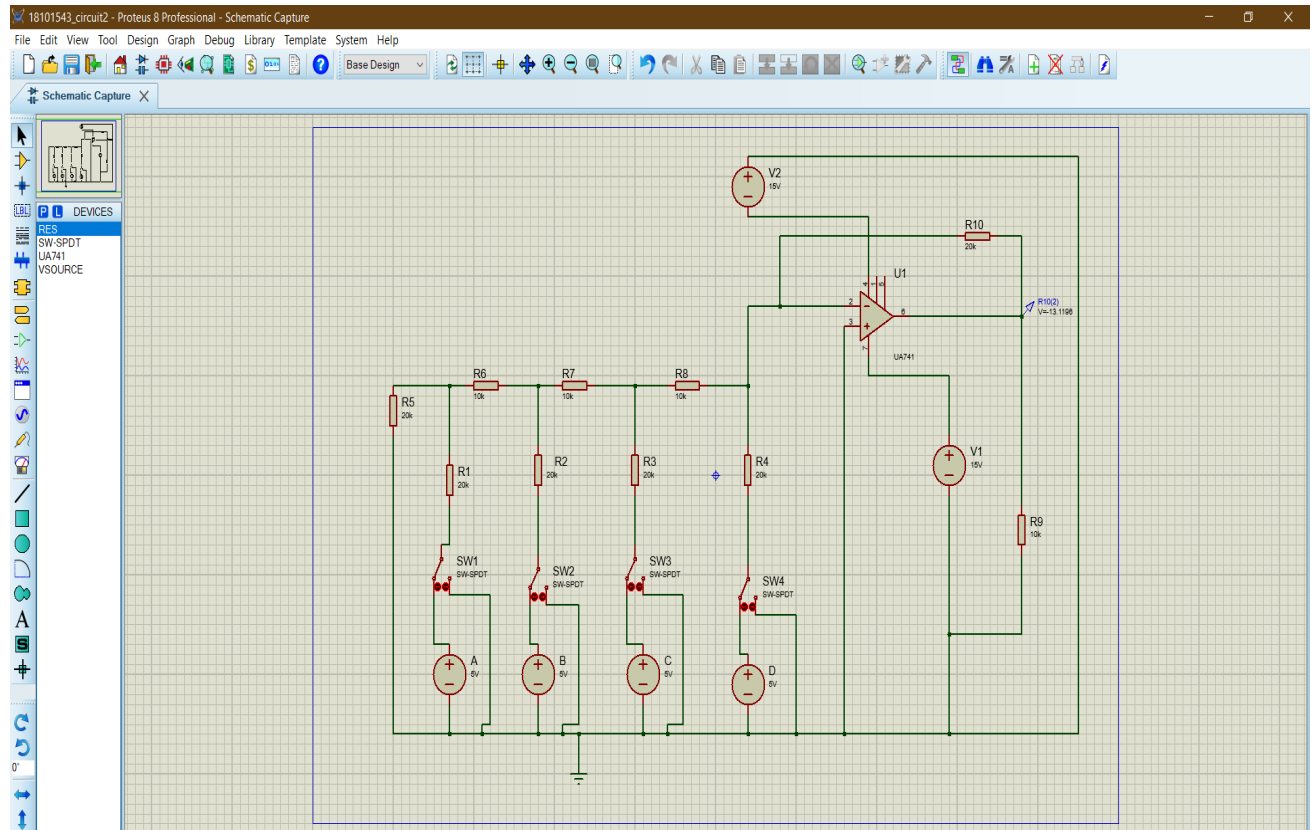

Ans. to the ques. no. 2-02

Here full step size of the circuit is 15. We get this by plotting the values in a graph by plotting the values in a graph for both the circuits.

Ans. to the ques. no. 2-03

Resolution is 1V for the LSB of the 4 bit option.



Ans. to the ques. no. 9-04

Here, my id is = 18101543. So, sum of last 2 digits ~~are~~ is  $(4+3)=7$ . So, high input is 7. So, from circuit 2 by using 7v as high input we get these outputs:-

Input Configuration	D	C	B	A	output Voltage, $V_o(V)$
1	0	0	0	0	0.0049
2	0	0	0	7	-0.87
3	0	0	7	0	-1.74
4	0	0	7	7	-2.61
5	0	7	0	0	-3.49
6	0	7	0	7	-4.36
7	0	7	7	0	-5.24
8	0	7	7	7	-6.11
9	7	0	0	0	-6.99
10	7	0	0	7	-7.86
11	7	0	7	0	-8.74
12	7	0	7	7	-9.61
13	7	7	0	0	-10.49
14	7	7	0	7	-11.36
15	7	7	7	0	-12.24
16	7	7	7	7	-13.11

Ans. to the Ques. no. 8-06


for the 1st circuit the output is a staircase waveform and each step being roughly  $0.5\text{ V}$  each. the ~~aa~~ output current  $i_{\text{aVref}}$ . So, when the  $V_{\text{ref}}$  is increased or decreased  ~~$V_{\text{ref}}$  is on~~ the step size and full size output will change proportionally.



ID-18101543

SP181818 p-4

Graph for circuit 1

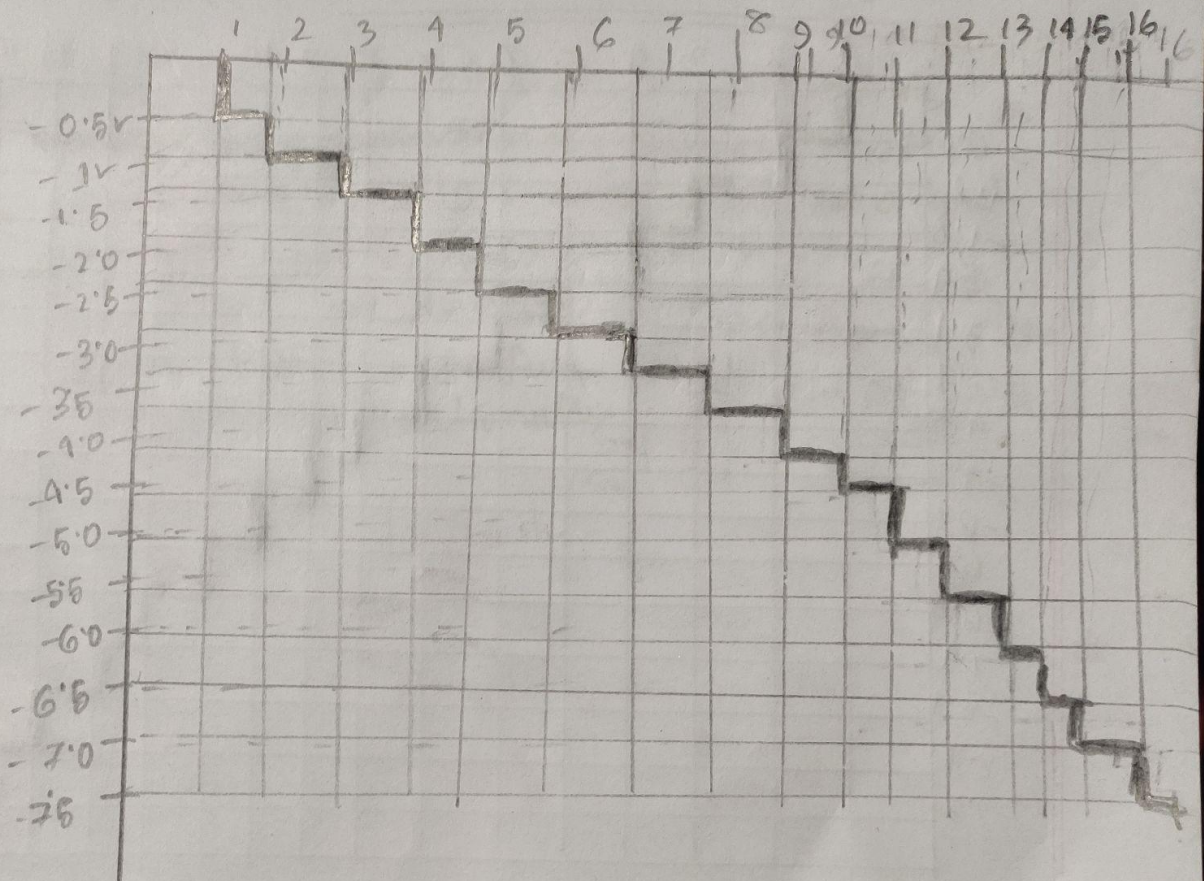

ID-18101543

SP310181 P-5

Graph for circuit 2:

